



K23U 1946

Reg. No. :

Name :

**II Semester B.C.A. Degree (CBCSS – OBE – Regular/Supplementary/
Improvement) Examination, April 2023
(2019 Admission Onwards)
Core Course
2B02BCA : DIGITAL SYSTEMS**

Time : 3 Hours

Max. Marks : 40

PART – A

(Short Answer)

Answer **all** questions.

(6×1=6)

1. If A and B are the inputs of a half adder, the sum is given by _____, while the carry is given by _____.
2. _____ is a digital circuit that is capable of storing only a single bit.
3. The primary memory of a personal computer consists of both _____.
4. According to Boolean law : $A + 1 =$ _____.
5. A De-multiplexer is a combinational circuit that has _____ input line and _____ output lines.
6. BCD stands for _____.

PART – B

(Short Essay)

Answer **any 6** questions.

(6×2=12)

7. Convert $(1973)_{10}$ to the hexadecimal number system.
8. What do you mean by ASCII ?
9. Describe AND and OR gate with Graphic Symbol, Truth Table.

P.T.O.

K23U 1946



10. Write a short note on decoder.
11. Briefly explain the master slave arrangement of flip flops.
12. State and prove De Morgan's Law.
13. What is a shift register ?
14. What is EPROM ?

PART – C

(Essay)

Answer any 4 questions.

(4×3=12)

15. Compare multiplexers and demultiplexers.
16. Describe the procedure involved in K-Map technique for reducing boolean expression with a suitable example.
17. Prove that $ABC + ABC' + AB'C + A'BC = AB + AC + BC$.
18. How will you calculate 1's complement and 2's complement ? Explain with an example.
19. Write a short note on ripple counter.
20. What do you mean by flash memory ?

PART – D

(Long Essay)

Answer any two questions.

(2×5=10)

21. Write a note on parity generators/checkers.
 22. Explain SOP and POS Minimization with examples.
 23. Compare and contrast the construction and working of RS and JK flip flops.
 24. What are shift registers ? Draw and explain bidirectional shift registers.
-