



K20U 0347

Reg. No. : .....

Name : .....

**II Semester B.C.A. Degree (CBCSS – Supple./Improv.)**

**Examination, April 2020**

**(2014-2018 Admissions)**

**CORE COURSE**

**2B02 BCA : Digital Systems**

Time : 3 Hours

Max. Marks : 40

**SECTION – A**

Answer **all** questions. **Half** mark **each** :

1. a) \_\_\_\_\_ waveform is one that repeats itself at a fixed interval.
- b) \_\_\_\_\_ is the unit of measurement of frequency.
- c) Name the IC with AND-OR logic.
- d) A diagram of input and output waveforms showing time relationships is called \_\_\_\_\_.
- e)  $\triangleright$  in a flip-flop diagram is called \_\_\_\_\_.
- f) Combination of binary digits that represent numbers, letters or symbols are called \_\_\_\_\_.
- g) Write an invalid bit combination in excess-3 code.
- h) Modulus-10 Johnson counter requires \_\_\_\_\_ number of flip-flops.

**SECTION – B**

Answer **any 7** questions. **2** marks **each** :

2. What is multiplexing ?
3. Distinguish between encoder and decoder.
4. Draw a logic diagram to decode 1011 with active-low output.
5. State self-complementing property.
6. What is look-ahead-carry addition ?

P.T.O.



7. Draw the logic diagram and timing diagram of a gated D flip-flop.
8. What is mean by pulse-triggered flip-flop ?
9. Draw the logic diagram of a 2-bit asynchronous binary counter.
10. Explain DeMorgan's theorem.
11. Draw the circuit and truth table of an SR latch.

## SECTION – C

Answer **any 4** questions. **3** marks **each** :

12. Simplify the following expressions using Boolean algebra.
  - a)  $(\bar{A} + B)C + ABC$
  - b)  $\bar{A}\bar{B}C(BD + CDE) + A\bar{C}$ .
13. Draw the logic diagram of a decimal keyboard encoder.
14. Perform the following binary operations.
  - a)  $10001 - 1101$
  - b)  $1101 \times 1011$
  - c)  $1111 \div 110$
15. Draw the logic diagram and timing diagram of an asynchronous decade counter.
16. Perform the following conversions :
  - a)  $(35.625)_{10}$  to binary
  - b)  $(1101.101)_2$  to decimal
  - c)  $723_8$  to hexadecimal.
17. Explain up/down counter in detail.

## SECTION – D

Answer **any 2** questions. **5** marks **each** :

18. Implement the functions of basic gates using universal gates.
19. Draw the logic symbol, logic diagram and truth table of half-adder and full adder.
20. Discuss about different types of shift registers.
21. Write a note on K-map. Minimise the following expression.
 
$$\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}BC\bar{D} + \bar{A}BCD$$