



K26U 0831

Reg. No. :

Name :

**Second Semester B.C.A. Degree (CBCSS – OBE – Supplementary)
Examination, April 2026
(2020 to 2023 Admissions)
Core Course
2B02BCA : DIGITAL SYSTEMS**

Time : 3 Hours

Max. Marks : 40

PART – A

Answer **all** questions. **Each** question carries **one** mark.

1. What is the 2's complement of $(11100)_2$?
2. Convert (125) decimal to binary.
3. Draw the logic diagram of NAND gate.
4. Give the result of A.A.
5. What is the truth table for half adder ?
6. What is the purpose of K-map ?

(6×1=6)

PART – B

Answer **any six** out of eight. **Each** question carries **two** marks.

7. Convert 131.5625 to binary.
8. a) 111011×11010
b) Subtract 11011 from 10110 using 1's complement.
9. State De-Morgan's theorem.
10. What is BCD ?
11. What is D flip-flop ? Write its characteristic table.
12. Simplify $A(A + B)$.
13. What is a decoder ?
14. Draw a 3 – variable K-map with squares indicating min terms.

(6×2=12)

P.T.O.



PART – C

Answer **any four** out of six. **Each** question carries **three** marks.

15. Convert :

- a) $(545.375)_{10}$ to octal.
- b) $(2890)_{10}$ to hexadecimal.
- c) $(232.2)_8$ to binary.
- d) $(64AC)_{16}$ to decimal.

16. Simplify using K-map.

$$F(A, B, C, D) = \pi M(1, 3, 5, 7, 13, 15)$$

Draw the logic circuit using AND-OR gate.

17. Explain the universal property of NOR gates with diagrams.

18. Explain 3-bit asynchronous counter.

19. Explain the parity generators/checkers.

20. What is the difference between a synchronous counter and asynchronous counter ?

(4×3=12)

PART – D

Answer **any two** out of four. **Each** question carries **five** marks.

21. Explain up/down synchronous counter.

22. Draw the logic circuit for the simplified form of expression.

$$F = AB + AC' + C + AD + AB'C + ABC$$

23. Explain :

- a) Number system
- b) Code converter.

24. Explain multiplexers and demultiplexers with diagram.

(2×5=10)